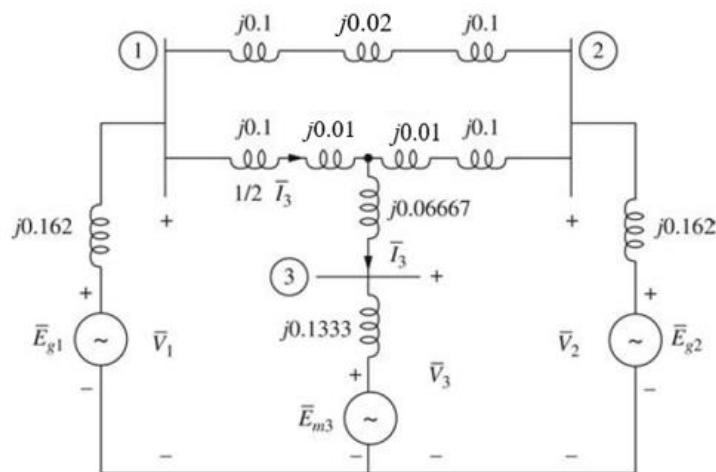


EEE352 Tutorial 1 Answers

NB: Please note that these are only the answers to the questions, the working has no been included. Use them as guidance only.

Q1: Equivalent reactance diagram:



Per-unit positive-sequence reactance diagram

Q2:

- (a) VR = 45.9%
- (b) At 50 Hz:
 $V_T = 11 \text{ kV}$
 $S = 100 \text{ MVA}$
- (c) AT 50 Hz:
VR = 45.9%

Q3:

$$A = D = 0.9918 \angle 0.0999^\circ \text{ per unit}$$

$$B = 51.1 \angle 82.11^\circ \Omega$$

$$C = 3.216 \times 10^{-4} \angle 90.033^\circ \text{ S}$$

(a) 0.9 lagging

$$V_S = 151.3 \angle 12.98^\circ \text{ kV}_{\text{LN}} = 262 \text{ kV}_{\text{LL}}$$

$$\text{VR} = 21.2 \%$$

(b) Unity

$$V_S = 136.6 \angle 17.2^\circ \text{ kV}_{\text{LN}} = 236.6 \text{ kV}_{\text{LL}}$$

$$\text{VR} = 9.43 \%$$

(c) 0.9 leading

$$V_S = 118.9 \angle 19.1^\circ \text{ kV}_{\text{LN}} = 205.9 \text{ kV}_{\text{LL}}$$

$$\text{VR} = -5.6\%$$